

LEDs for General Illumination – A Disruptive Technology

Fred Greenfeld
Intersil Corporation


General Purpose Lighting – Where We are Today

- Commercial/Industrial
 - Factory Lighting
 - Street Lamps
 - Types
 - Mercury Vapor
 - Sodium (High/Low Pressure)
 - Other High Intensity Discharge (HID)
 - Fluorescent



Courtesy Wikipedia

High Pressure Sodium Lamp

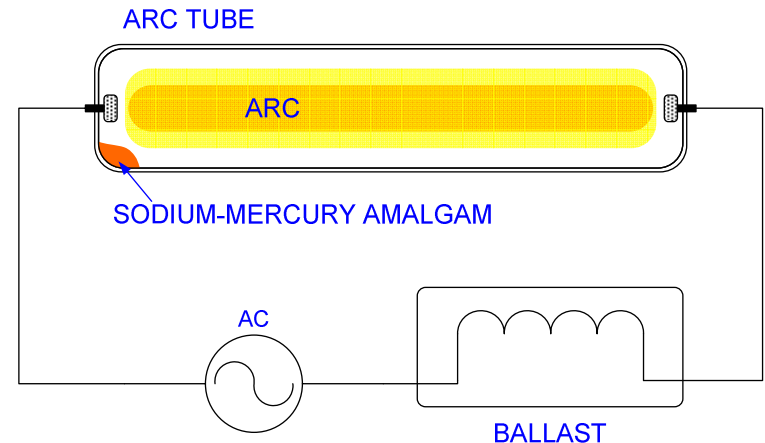

General Purpose Lighting Today

- Residential
 - Incandescent
 - Tungsten, Halogen
 - Compact Fluorescent
 - Fluorescent




Photos courtesy OSRAM SYLVANIA

General Purpose Lighting Today

- Terminology and Performance
 - Efficiency/Efficacy
 - Cost of operation
 - Efficacy – Measure of output useful for illumination determined by the sensitivity of the human eye
 - Incandescent – 2.6% luminous efficacy, 100W tungsten [1]
 - Mercury Vapor - < 6% (coated) [8]
 - Compact FL – < 8.8 % luminous efficacy, 5-24W [1]
 - Fluorescent – < 15.2% luminous efficacy [1]
 - HP Sodium – 22% [1]
 - LP Sodium – 27% [1]

General Purpose Lighting Today

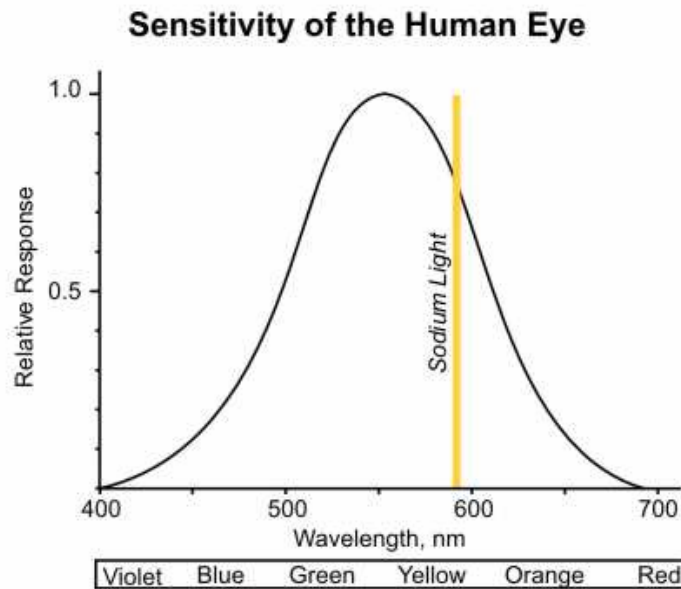- Characteristics
 - Color
 - Chromacity/Color temperature
 - How close is output to natural sunlight at noon?



Human Eye Sensitivity and Low Pressure Sodium Spectrum⁵

General Purpose Lighting Today

- Characteristics (cont'd)
 - Warm-up
 - How long before intensity/color is steady state?
 - Mercury Vapor
 - Sodium
 - » LPS/SOX low pressure (600nm)
 - » HPS/SON
 - Compact Fluorescent/Fluorescent
 - Reliability/Life Expectancy/Disposal
 - Service/Maintenance costs
 - Mercury Vapor – 24,000 hours (50% output @ 5 years)
 - LPS/SOX Sodium - 18,000 hours
 - Incandescent - 1000 hours
 - Disposal (toxic/reactive)

Power Requirements

- Conventional Lighting
 - AC Power
 - Off-line AC mains (120/240/415 VAC, etc.)
 - Low voltage AC systems (12 VAC)
 - Architectural lighting
 - Resistive (incandescent), or
 - Ballasted
 - Starter
 - Limits current
 - Improves Power Factor

White LEDs

- Characteristics

- Efficiency/Efficacy

- Up to 22%⁴
 - Single proto-type LED 1000 lumens (60W tungsten = 850 lm)⁶

- Color

- Similar to Fluorescent (NUV/UV emitter plus phosphor)
 - Cool, Neutral, Warm
 - Color can be further adjusted by interspersing colored LEDs

- Warm-up


- None

- Reliability/Life Expectancy

- Catastrophic failure rare
 - Reduction of intensity
 - Color shift
 - 50,000 hour life expectancy



Courtesy Cree

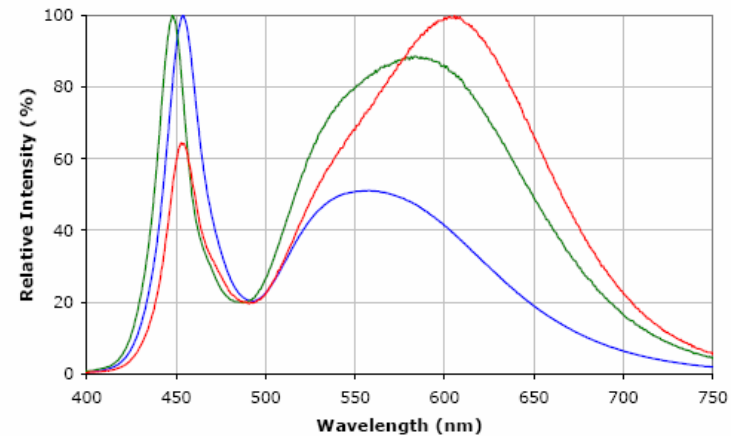

Courtesy Cree


White

White LEDs

- Characteristics
 - Cost
 - A quickly moving target
 - Still several times the cost of equivalent fluorescent
 - Adopted in high maintenance cost locations

Power Requirements

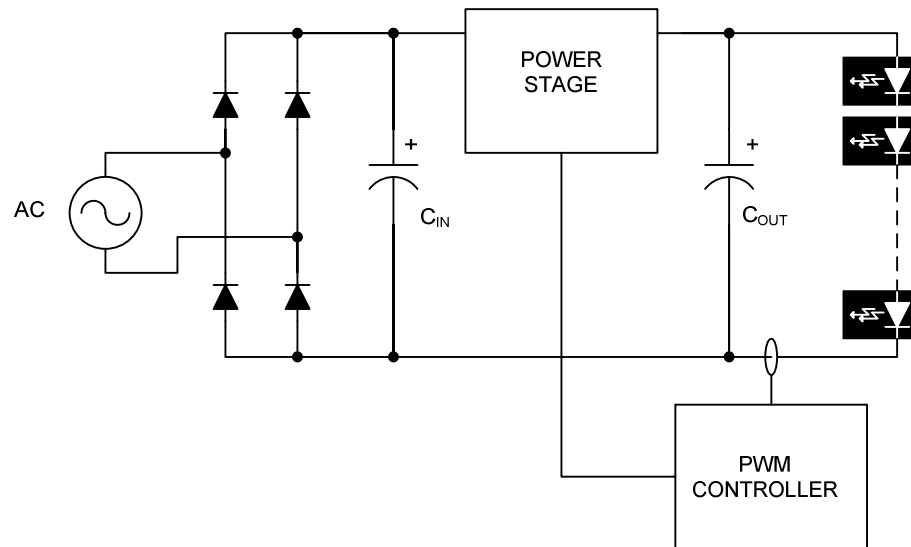- LEDs
 - Low voltage DC
 - 3.5 V @ 350 – 1000 mA (typ.)
 - Up to 107 lumens (production)
 - Requires a current source, not a voltage source





LED Driver Block Diagram

Power Quality


– Power Factor – A Quick Review

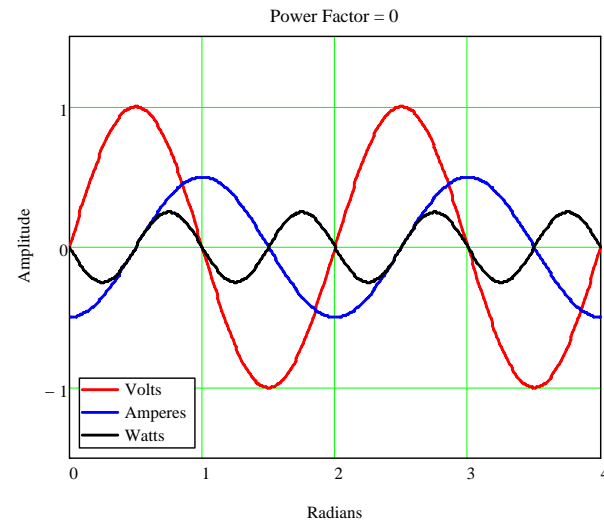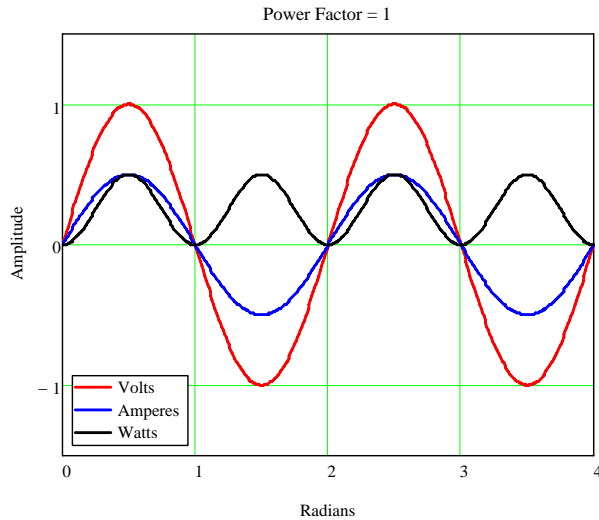- $PF = \text{Real Power} / \text{Apparent Power} = \text{Watts} / (V_{\text{rms}} \times A_{\text{rms}})$
- Dimensionless ratio ranging from 0 to 1
- If V and A are not in phase, or if system is non-linear (rectified input), then PF will be reduced
 - Real Power + Reactive Power/Harmonics



Power Supply w/o PFC

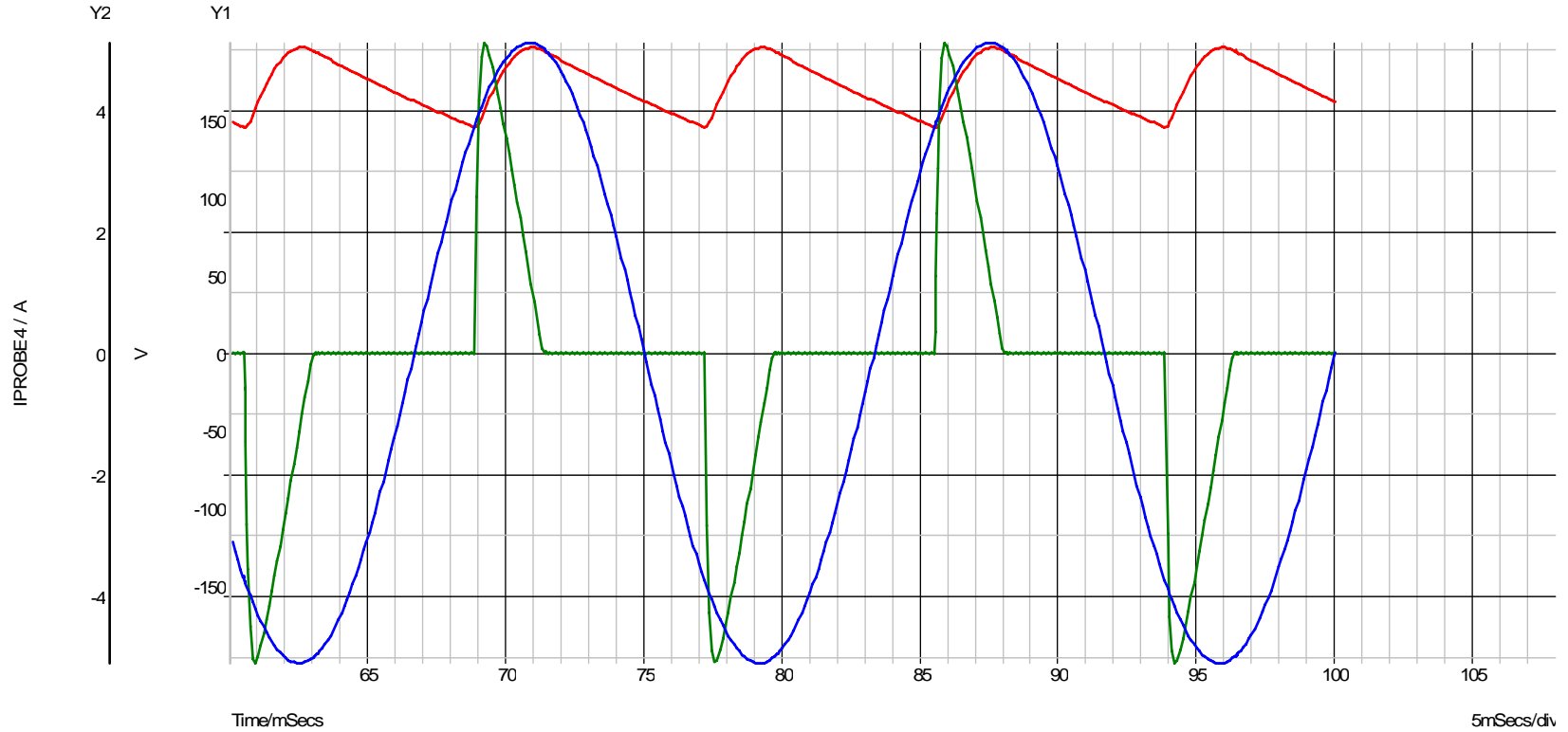- Power Factor in an Uncorrected AC Input P/S
 - PF = 0.55 to 0.65



- Input Current
- Input Voltage
- Input Capacitor Voltage

THE NUMBER ONE SOURCE FOR HIGH PERFORMANCE ANALOG

Power Factor Facts

- Power Factor/Harmonic Content
 - Why is this important?
 - Only Real Power is capable of doing work
 - Low PF requires higher currents to deliver equal power
 - Low PF means higher generation and transmission costs
 - Non-PFC power converters reduce any energy efficiency gains by 1-PF
 - Cause higher currents in neutral branch (3 ϕ)


- Is PFC Actually Required?
 - Europe specifies harmonic content limits (IEC61000-3-2 A,C, D)
 - Class C applies to lighting >25W
 - Class D applies to lighting <25W (mA/W)
 - Class A/D applies to all converters
 - Most are anticipating regulatory requirements

Power Factor Facts

- What is the Energy Impact?
 - LED vs. CFL vs. Incandescent
 - PFC vs. non-PFC
 - ~110 Million US households (US Census)
 - A typical US household has 50-100 light bulb sockets⁷
 - Do the math...
- What is the cost of adding PFC?
 - Essentially free

Adding PFC

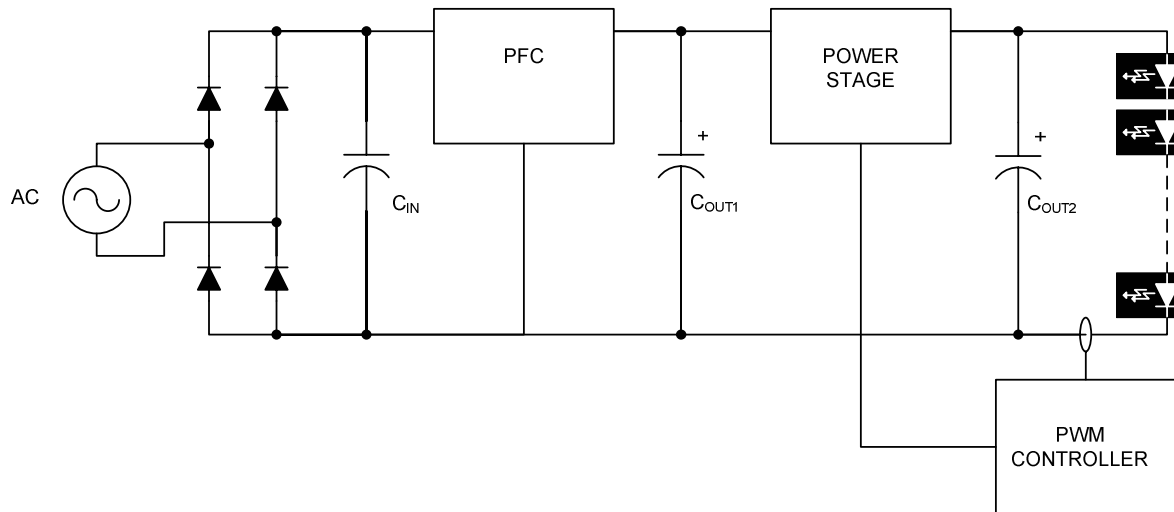- Power Factor Correction (PFC)
 - How is PFC provided?
 - Could use 2-stage approach, but.....




Adding PFC

- Power Factor Correction (PFC)
 -2-stage PFC is costly (not free) and unnecessary
 - To get high PF, the load reflected to the AC line needs to appear resistive
 - $I = V/R$ or $I \propto \kappa V$
 - For an inductor, $\Delta I = \Delta T * V/L$
 - where $\Delta T = T_{ON}$ is the time V is applied across L
 - If T_{ON} is a constant
 - then $\Delta I \propto \kappa V$
 - If operating in DCM (or CrCM), then $\Delta I = I_{PEAK}$, and we have $I_{PEAK} \propto \kappa V$
 - If I_{PEAK} is averaged, then $I \propto \kappa V$
 - has same form as a resistance
 - Can do this in a single stage converter with
 - Constant On-time control
 - DCM or CrCM operation
 - Differential EMI filter

Adding PFC

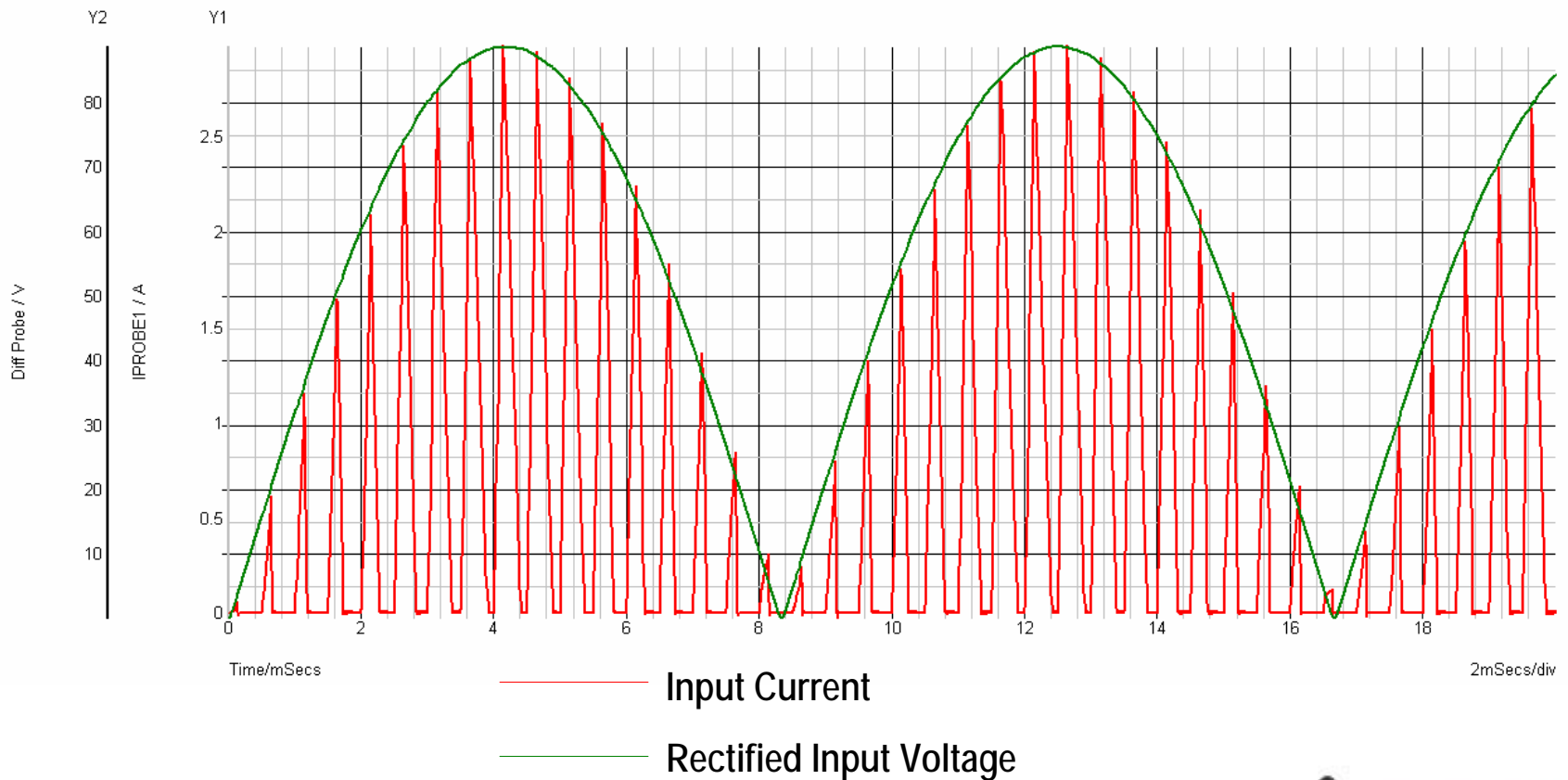- Single- stage PFC
 - Constant On-Time
 - DCM (fixed frequency)/CRCM (variable frequency) operation




Adding PFC

- Single-stage PFC to output
 - Existing Voltage-Mode PWM controllers are constant frequency
 - Support DCM operation
 - Many PFC controllers are available
 - Support CrCM operation
 - How do you get Constant On-Time control?
 - T_{ON} must be essentially constant over an AC half-cycle
 - Very low BW control loop
 - < 100 Hz
 - Applicable to virtually any hard-switched PWM topology
 - Boost
 - Flyback
 - SEPIC
 - CUK
 - Forward
 - Buck-Boost
 - Buck
 - Bridge (half and full)

Adding PFC

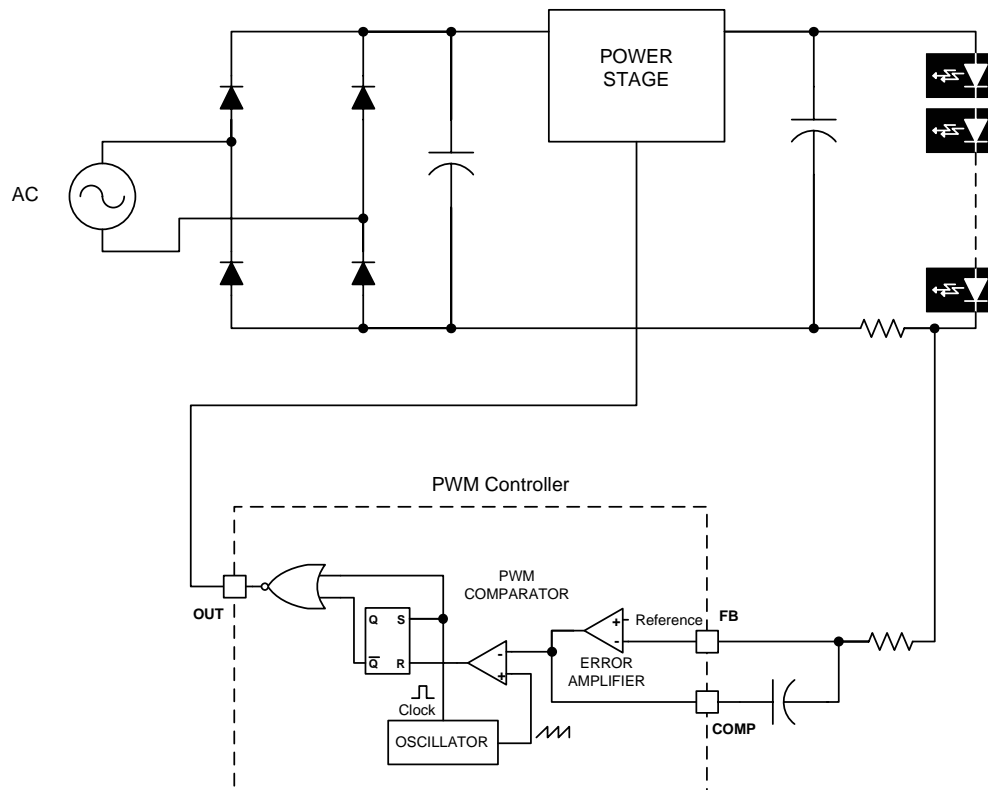- Single-stage PFC to output (cont'd)
 - Control loop monitors output current
 - Simple Type 1 integrator



Selecting the Topology

- What topology to choose?
 - Is input to output isolation required?
 - Existing lighting does not require it – should LED lighting?
 - But some customers are asking for it
 - Industrial applications
 - Modular applications
 - Input to output voltage differential
 - Large differential between V_{IN} and V_{OUT} means narrow duty cycle
 - Typical when operating from AC to small LED string
 - Choose transformer based topology if duty cycle is too small
 - » However, input and output can have a common ground


Design Example

- Requirements

- $V_{IN} = 120/240 \text{ VAC (90-275VAC)}$
 - $V_{IN(\text{min, avg})} = 81 \text{ V}$
 - $V_{IN(\text{max, avg})} = 250 \text{ V}$
- 21 LED series string
 - $V_{OUT} = 21 \times 3.5 = 73.5\text{V}$
 - $I_{LED} = 350 \text{ mA}$
- Switching frequency < 140 kHz (FCC, CISPR)
 - Use 100 kHz
- Want to choose cheapest voltage step-down topology
 - Any of the transformer-based topologies
 - Buck
 - Buck-Boost
 - CUK
 - SEPIC

Design Example


- The SEPIC converter

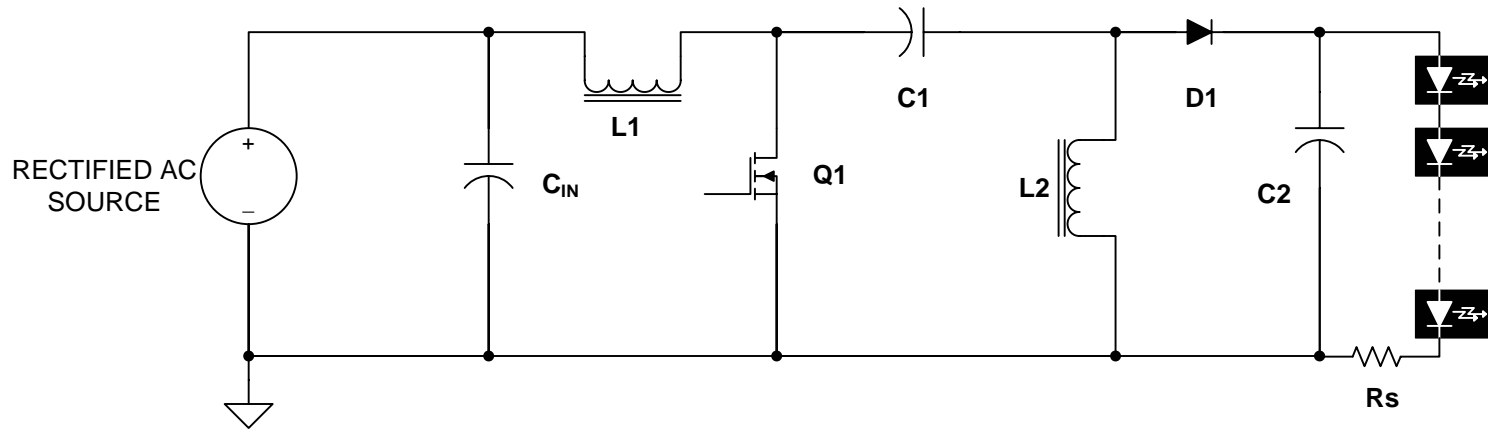


- Steady State Operation

- Average inductor (L1, L2) voltage must be zero
- $\therefore V_{C1}$ must be V_{IN}
- Average capacitor (C1) current must be zero
- $\therefore I_{OUT}$ must be $I_{L2(avg)}$

Time Interval Review

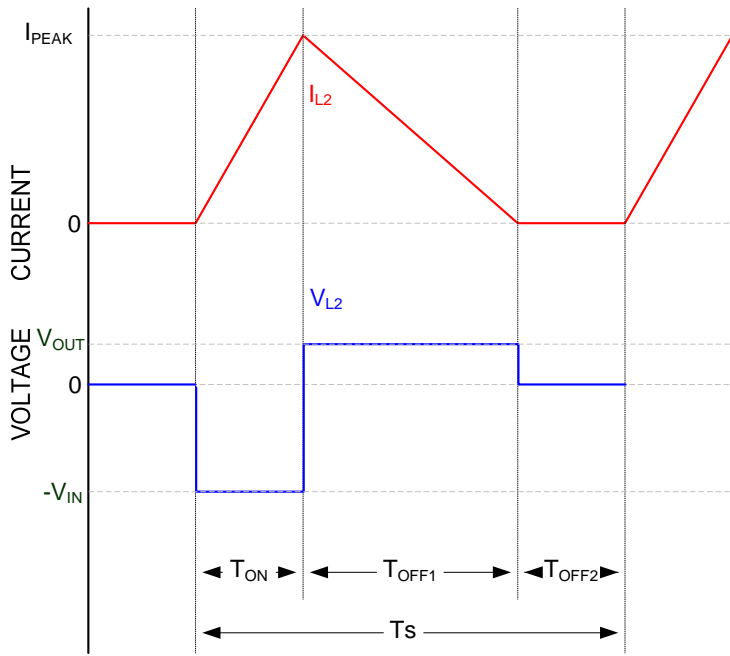


DCM Timing
(Fixed Frequency)

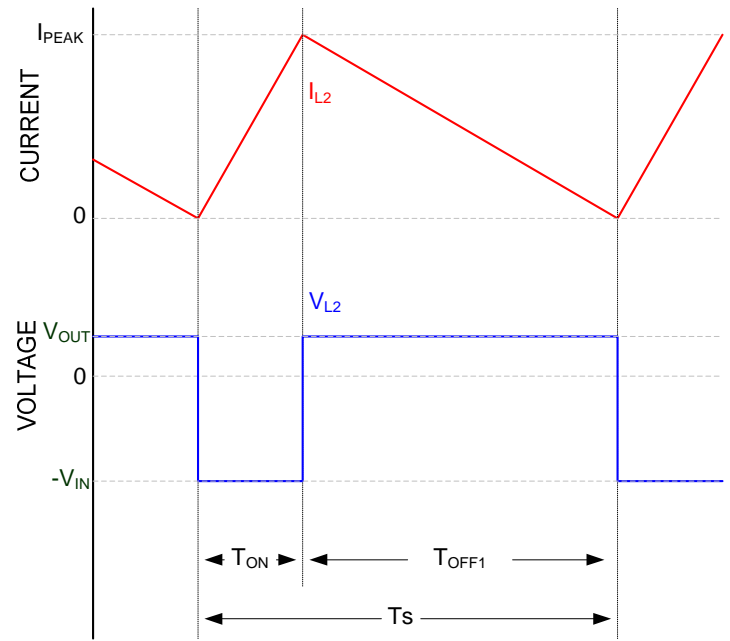

CrCM Timing
(Variable Frequency)


Design Example - SEPIC

- The SEPIC converter - T_{ON}

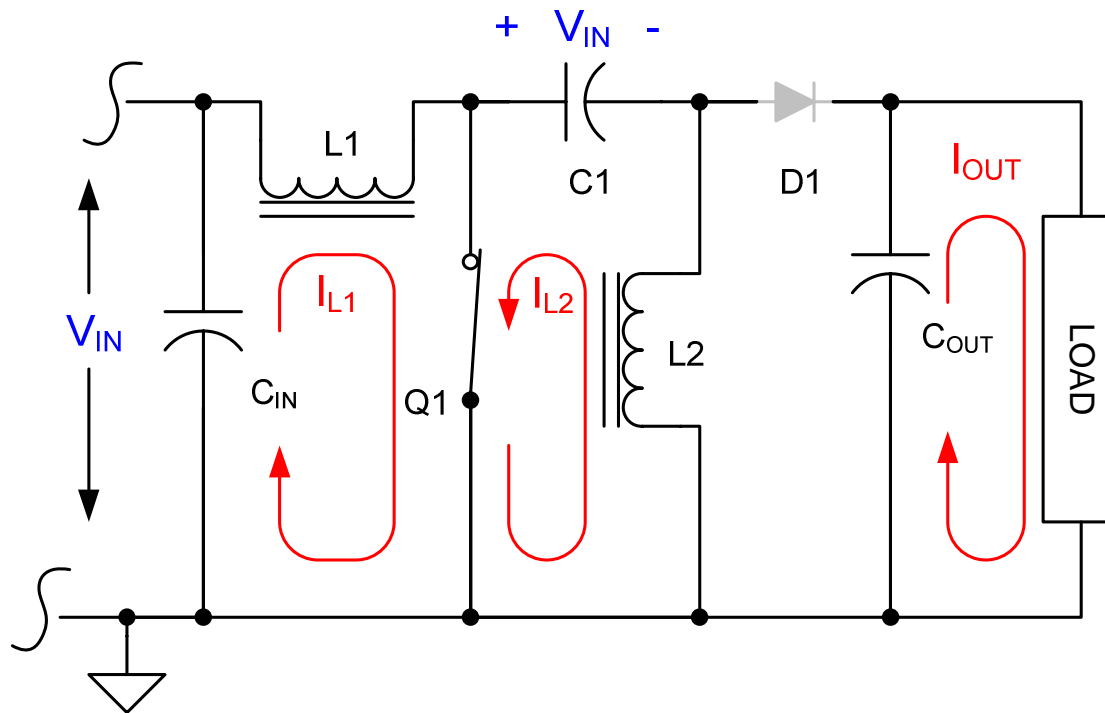


Design Example - SEPIC

- The SEPIC converter – T_{OFF1}

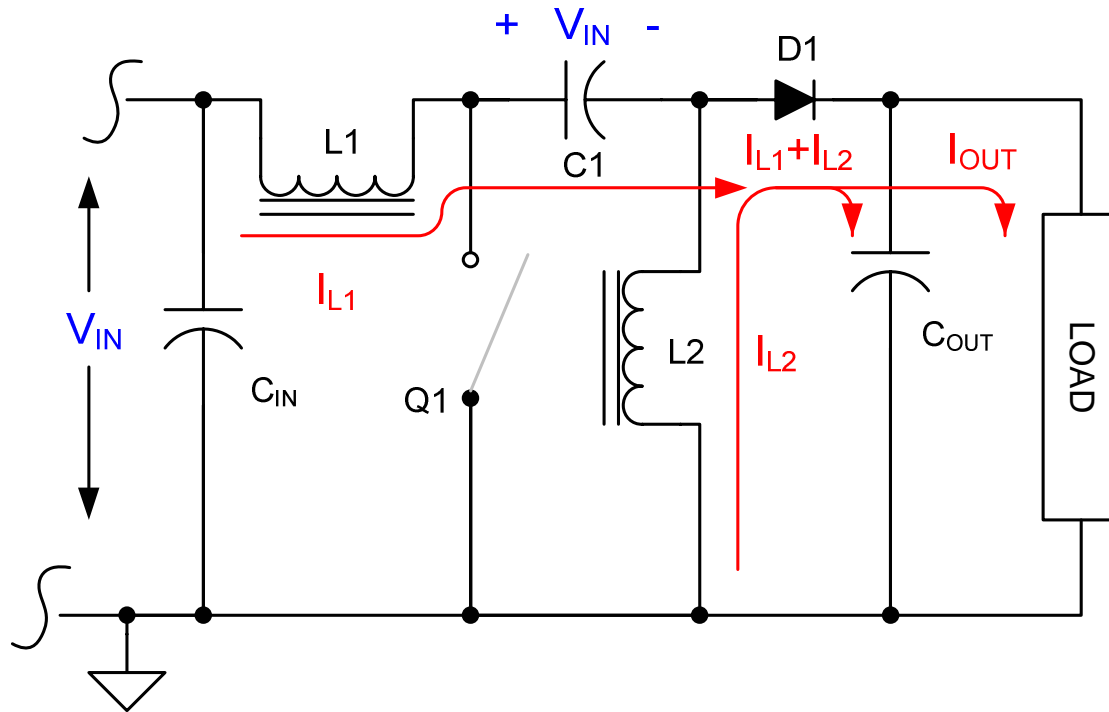

Design Example - SEPIC


- The SEPIC converter – T_{OFF2}

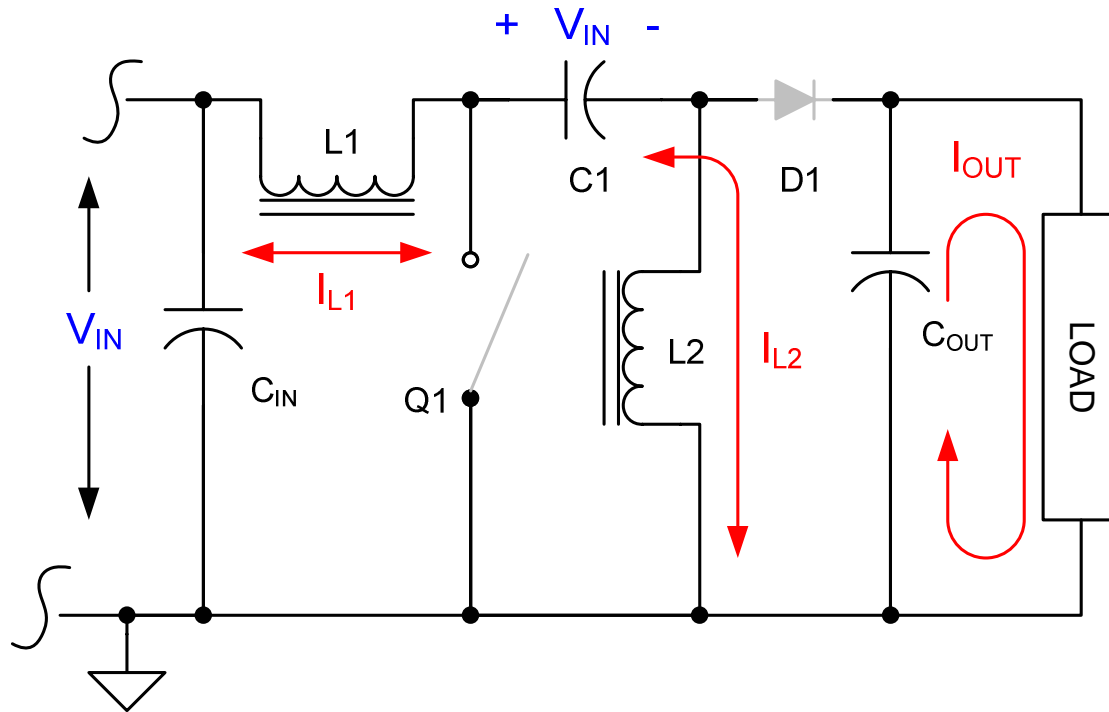

Design Example - SEPIC

- The SEPIC converter – T_{OFF2}
 - I_{Lx} not zero during T_{OFF2} due to charge balancing in coupling capacitor C1
 - Want to keep I_{C1} positive
 - Or it charges CIN and distorts input current
 - $L1 \gg L2$
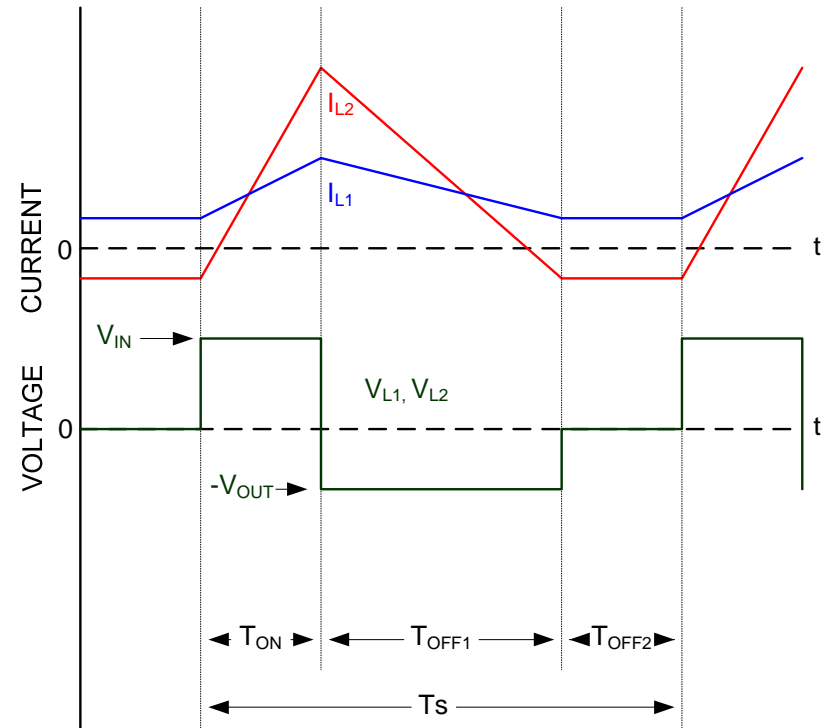
$$I_{C1(DC)} = \frac{L_1 I_{OUT}}{L_1 + L_2} \left(\frac{V_{IN} V_{OUT}}{\bar{V}_{IN}^2} - \frac{L_2}{L_1} \right)$$



Design Example - SEPIC

- Operation (cont'd)
 - For DCM operation
 - Worst case is at maximum duty cycle (min $V_{IN(PEAK)}$)

$$\frac{L_1 L_2}{L_1 + L_2} \leq \frac{\left(\frac{\bar{V}_{IN}}{V_{IN} + V_{OUT}} \right)^2 T_S V_{OUT}}{2I_{OUT}}$$

T_S = Switching Period

V_{IN} = Minimum Vrms peak voltage

\bar{V}_{IN} = Minimum V_{IN} Vrms average

- L1 selection has conflicting requirements
 - Large L1 reduces peak currents
 - Large L1 increases distortion at AC zero-voltage crossing which compromises PF

Design Example - SEPIC

- Operation (cont'd)
 - $V_{OUT}/V_{IN} \neq D/(1-D)$ due to DCM operation

$$T_{OFF1} = \sqrt{\frac{2T_S I_{OUT}}{\left(\frac{1}{L_1} + \frac{1}{L_2}\right) V_{OUT}}}$$


$$T_{ON} = \frac{V_{OUT}}{V_{IN}} T_{OFF1}$$

$$T_{OFF2} = T_S - T_{ON} - T_{OFF1}$$

Design Example - SEPIC

- Control Loop BW

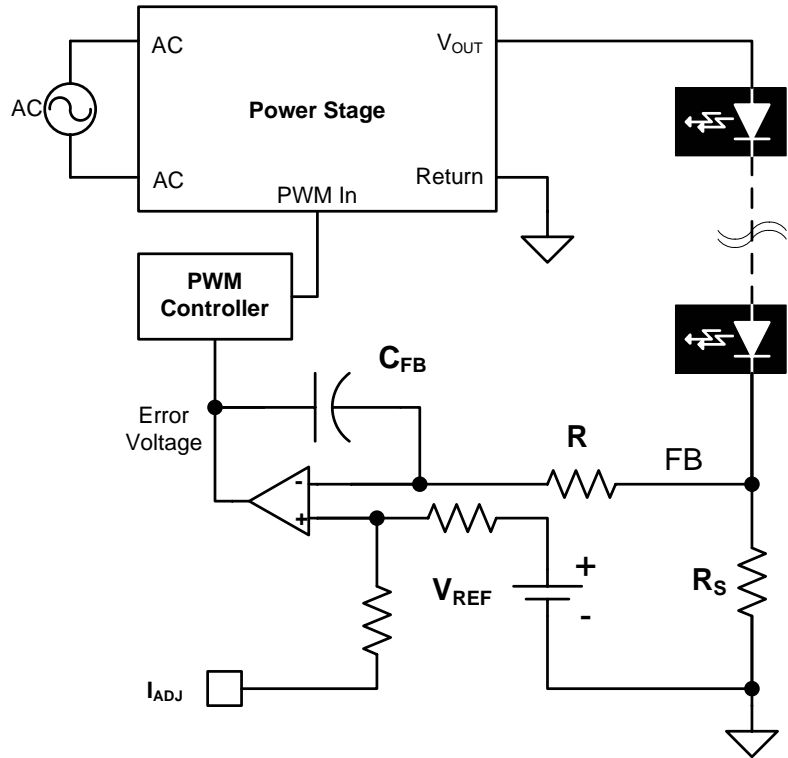
- $f_C = 1/2\pi RC_{FB} = 40$ Hz
- $C_{FB} = 0.1 \mu F$
- $R = 40.2 k\Omega$
- Valid for all topologies




Design Example - SEPIC

- Choose $L1 = 820 \mu\text{F}$
- Choose $L2 = 82 \mu\text{F}$
- What PWM controller to use?
 - Voltage mode
 - Cheap
 - ISL6745

Design Example – SEPIC (simulation)

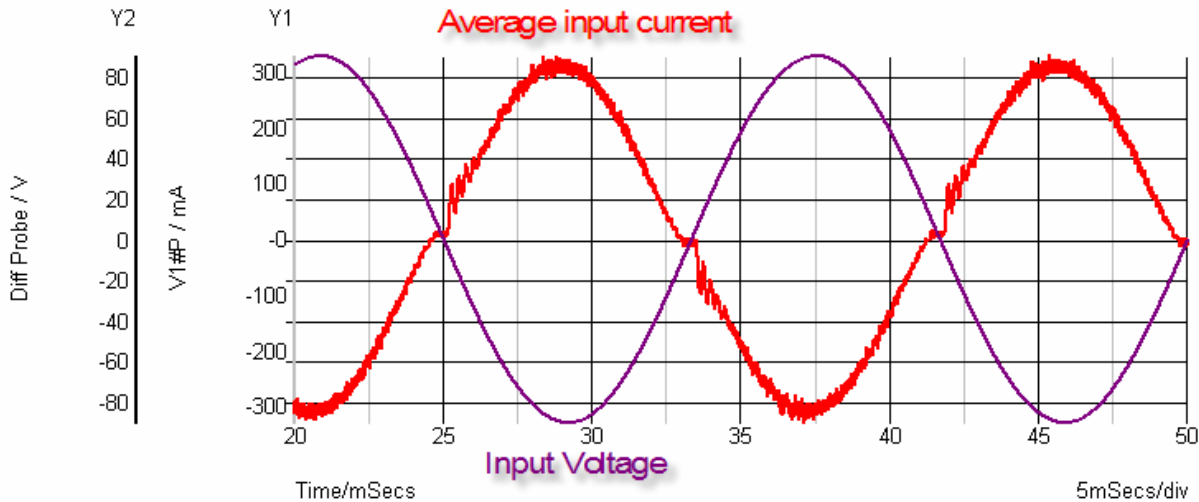


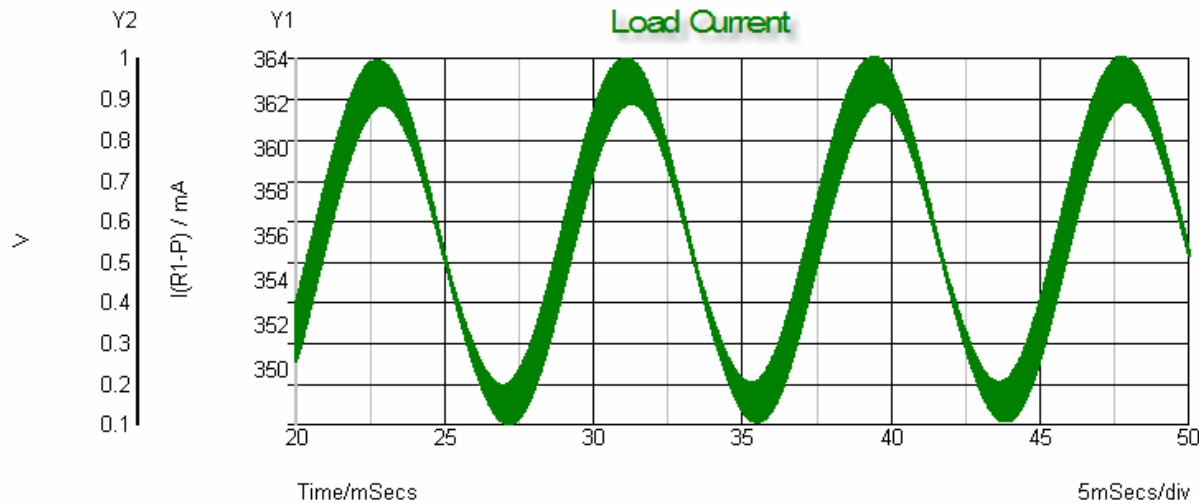
Typical input waveforms
(Voltage waveform intentionally shifted 180° for clarity)




Typical output waveforms
AC+DC current,
AC amplitude dependent on size of output capacitor

Design Example – SEPIC (experimental)

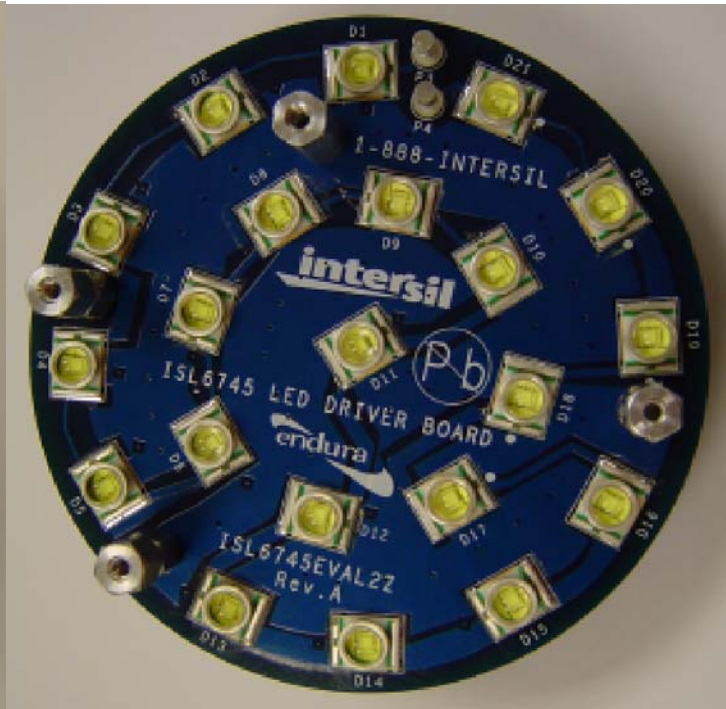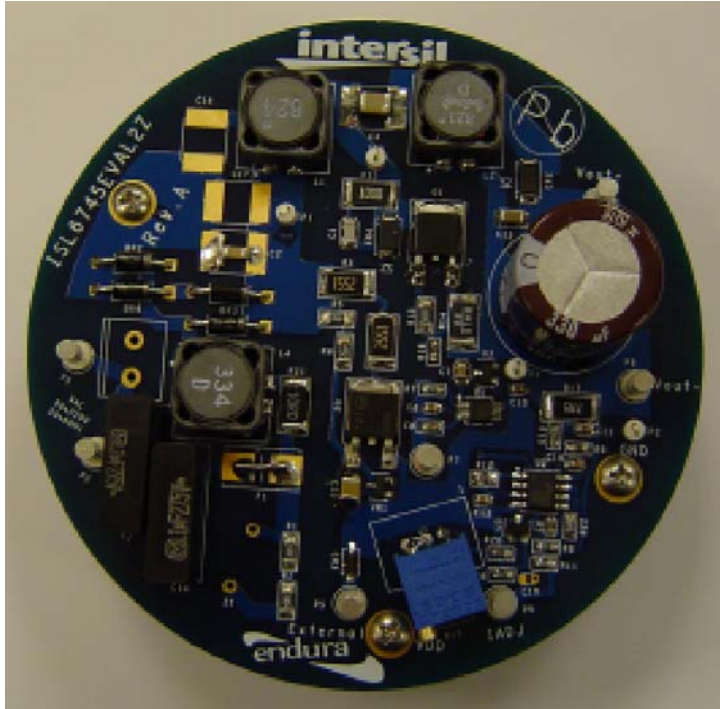
THE NUMBER ONE SOURCE FOR HIGH PERFORMANCE ANALOG



Design Example – SEPIC (experimental)

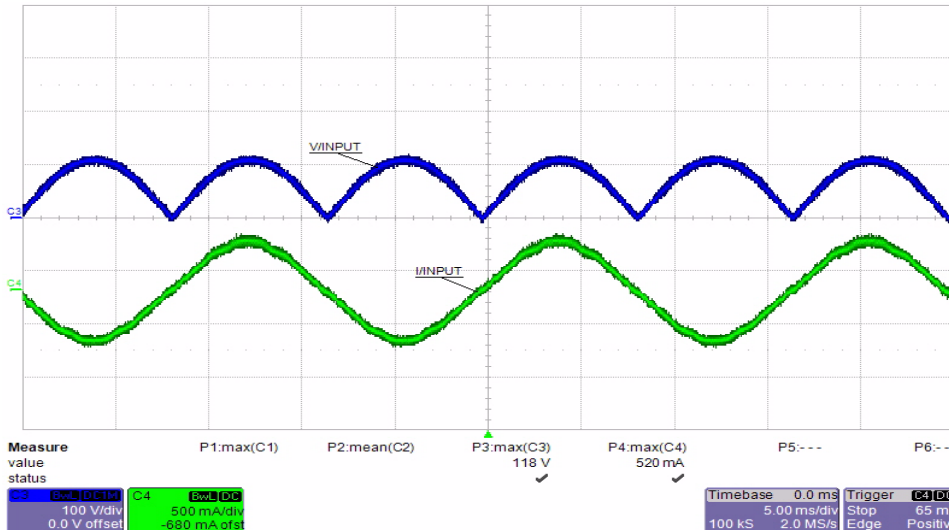


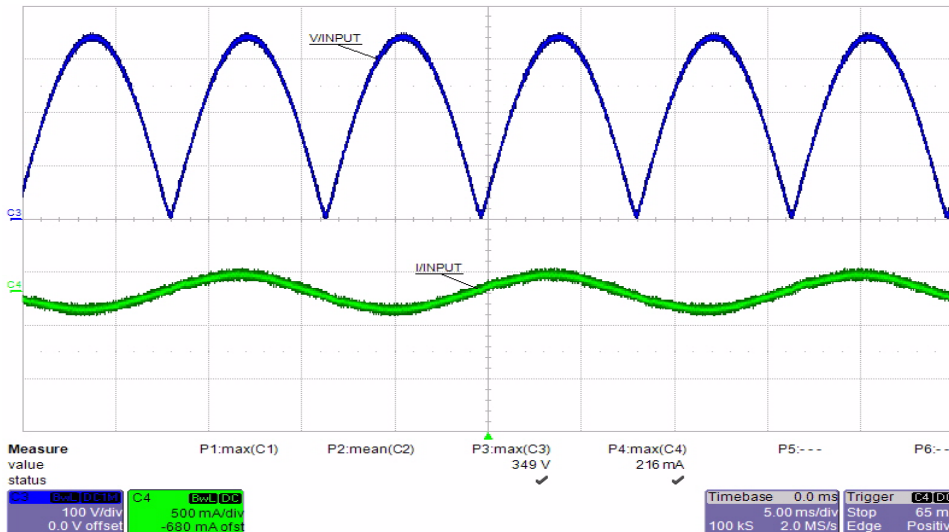Input waveforms:
 $V_{IN} = 80VAC$
 Rectified V_{in} (blue)
 100V/div
 Input current (green)
 500mA/div



Input waveforms:
 $V_{IN} = 240VAC$
 Rectified V_{in} (blue)
 100V/div
 Input current (green)
 500mA/div

Design Example – SEPIC (experimental)

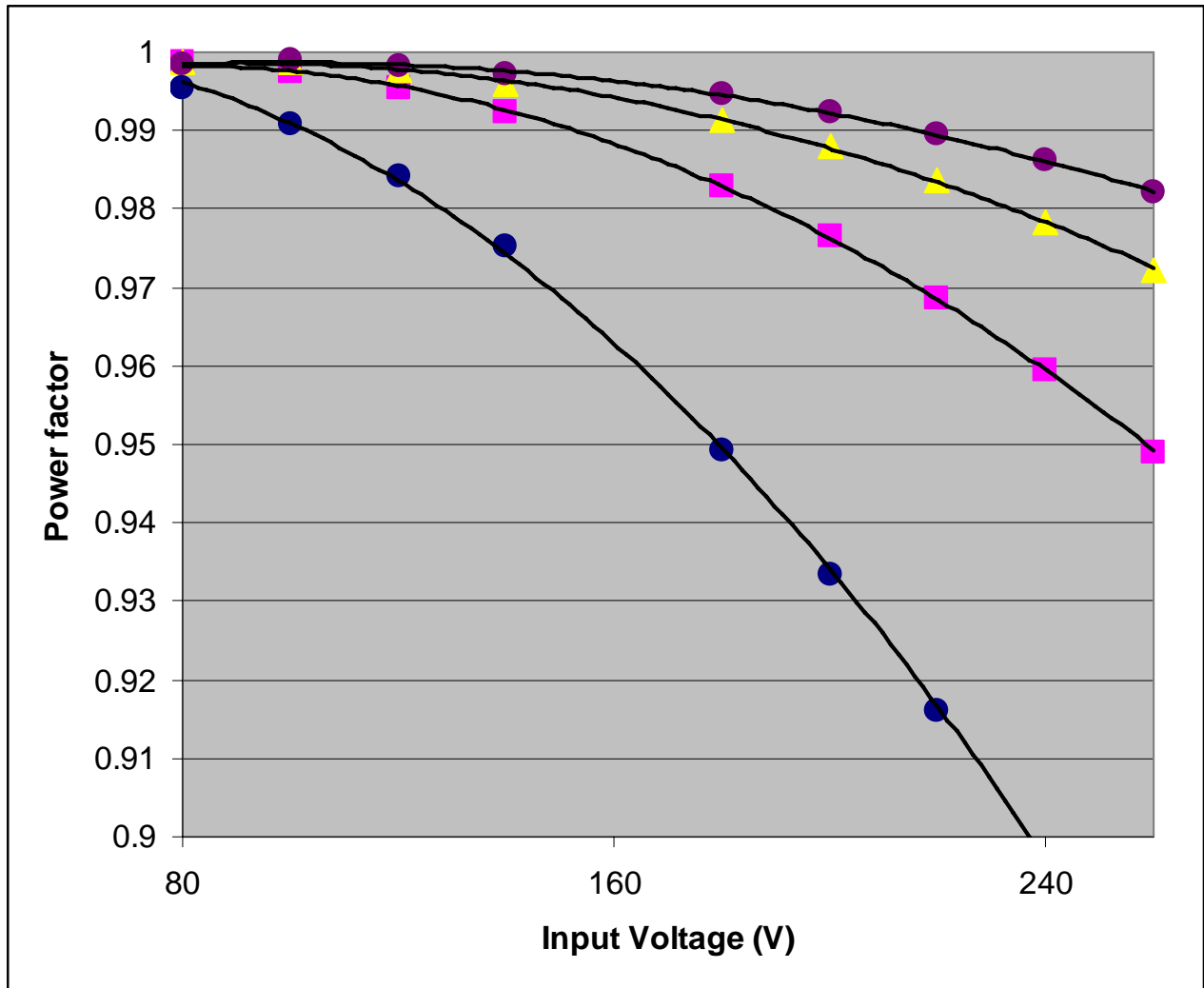


PF vs. Load and V_{IN}

Dimming LEDs

- Intensity dependent on current
- Color rendition also dependent on current
- Can use PWM techniques to turn LEDs on and off to modulate intensity rather than current modulation
 - But low end applications will likely modulate current only
- Strong industry desire to have LED fixtures compatible with incandescent wall dimmers
 - Constant output with varying AC amplitude
 - Variable output proportional to AC conduction angle

Multiple LED Strings

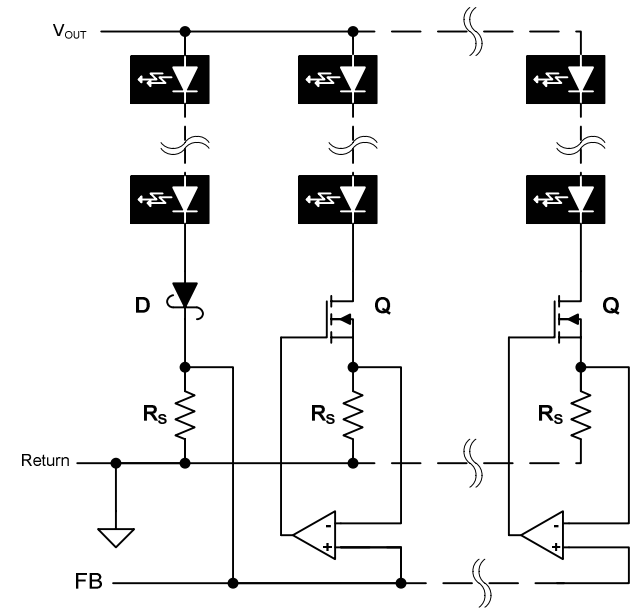- Industrial/Commercial applications can require multiple LED strings
 - Increased output
 - Fault tolerance
- How to control the current through each string?



Product Example

- 6" Can Light Replacement
 - LLF (division of CREE) Model LR6
 - 650 Lumens (~75W reflector flood)
 - 12W
 - Dimmable
 - PFC
 - Color corrected \$120 - \$144 (as of May 1, 2008)

Courtesy Cree

Conclusions

- White LEDs will become a significant, if not the dominant, light source for general illumination
- LED lighting products can be designed using readily available components
- Operating LED fixtures can have minimum impact on power quality

References

1. "LED or Neon? A Scientific Comparison", Thielen, Marcus, February 10, 2006
<http://www.signweb.com/index.php/channel/12/id/138/>
2. "The Great Internal Light Bulb Book, Part I", Klipstein, Donald L.
<http://freespace.virgin.net/tom.baldwin/bulbguide.html>
3. "Sodium Vapor Lamp", Wikipedia, retrieved May 1, 2008
http://en.wikipedia.org/wiki/Sodium_vapor_lamp
4. "CREE Achieves Highest Efficacy from a High-Power LED", CREE Press Release, September 13, 2007 http://www.cree.com/press/press_detail.asp?i=1189687350946
5. "The Low Pressure Sodium Lamp", Lamptech, September 20, 2003
<http://www.lamptech.co.uk/Documents/SO1%20Introduction.htm>
6. "Cree Achieves 1,000 Lumens from a Single LED", CREE Press Release, September 7, 2007 http://www.cree.com/press/press_detail.asp?i=1189169857943
7. "How Many Lightbulbs Does it Take to Change the World? One. And You're Looking At It", Fishman, Charles, retrieved May 1, 2008
http://www.fastcompany.com/magazine/108/open_lightbulbs.html
8. Osram Sylvania Product Information Bulletin, retrieved May 1, 2008
http://dafnwebpd.sylvania.com/os_filenet_pages/navview.asp?docid=003695698&Title=Product%20Information%20Bulletin&NAED=69453&doctyp=Document&wdth=600&hgth=450&Desc=CP103R3E